

## Chapter III(2): Balanced Three-Phase Systems.

### I. Introduction



Why three-phase systems?

- Electric energy is transported in three phases because a three-phase line dissipates less electrical energy than a single-phase line, reducing losses.
- Three-phase machines have better efficiency than single-phase machines and the price of the machines is directly linked to their mass (for equal power, a single-phase machine is one and a half times heavier than a three-phase machine.)
- A three-phase line is more economical than a single-phase line.
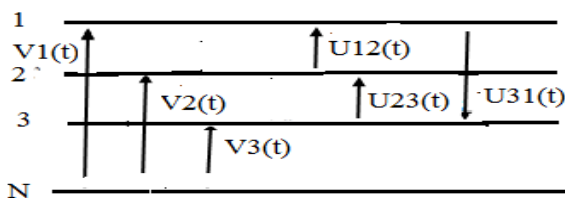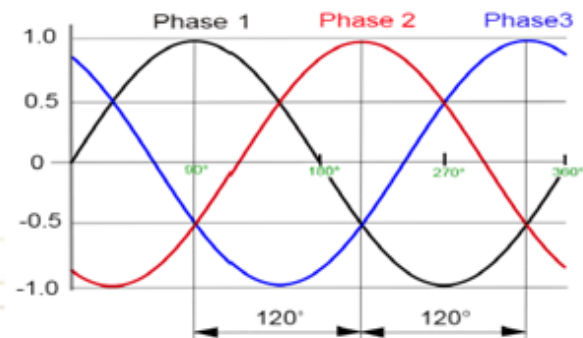
### II. Simple voltages and compound voltages

The most common type of polyphase sources is the three-phase source ; We consider:

- a source: EDF three-phase alternator •
- a load: three-phase receiver made up of 3 identical impedances •
- the lines: 3 identical wires called phases Ph and a wire called neutral N. •



#### Equations


We choose  $v_1(t)$  as reference voltage:

$$\begin{cases} v_1(t) = V\sqrt{2}\sin(\omega t) \\ v_2(t) = V\sqrt{2}\sin\left[\omega t - \frac{2\pi}{3}\right] \\ v_3(t) = V\sqrt{2}\sin\left[\omega t - \frac{4\pi}{3}\right] \end{cases}$$

$V_1, V_2, V_3$  are called simple tensions





$V_1 + V_2 + V_3 = 0$  Fresnel vectors
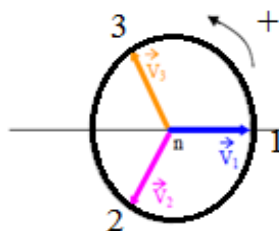
$$\begin{aligned} v_1 &\rightarrow \vec{V}_1 [V; 0] \\ v_2 &\rightarrow \vec{V}_2 [V; -2\pi/3] \\ v_3 &\rightarrow \vec{V}_3 [V; -4\pi/3] \end{aligned}$$




$(U_{12}, U_{23}, U_{31})$  : are called compound voltages:

$$\begin{aligned} U_{12} &= V_1 - V_2 \\ U_{23} &= V_2 - V_3 \\ U_{31} &= V_3 - V_1 \end{aligned}$$

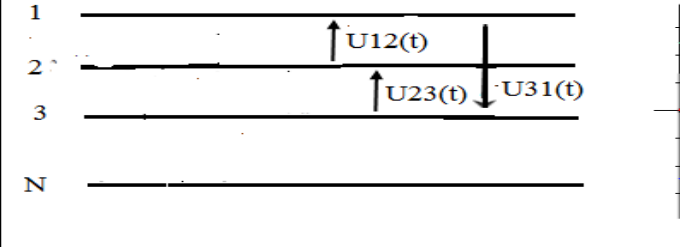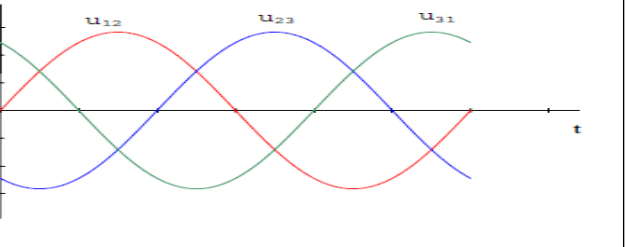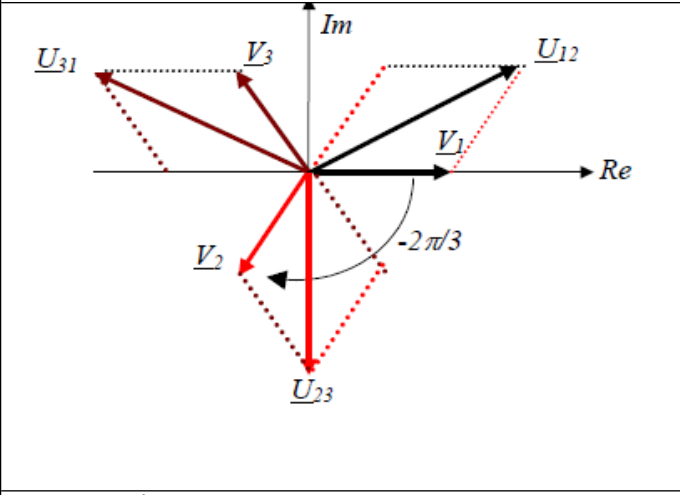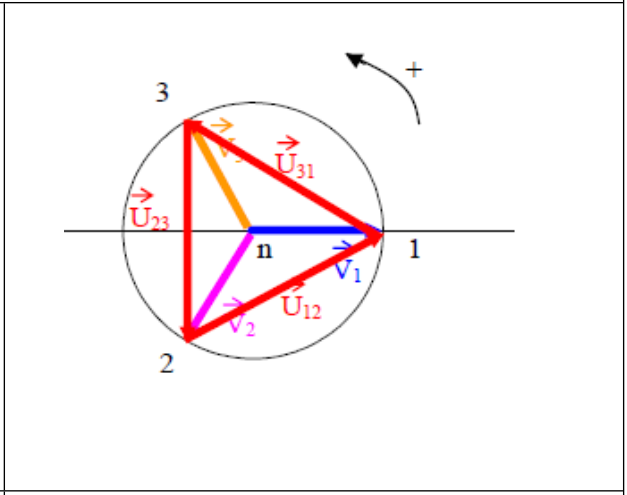	
	
$\begin{cases} U_{12}(t) = U\sqrt{2} \cdot \sin\left(\omega t + \frac{\pi}{6}\right) \\ U_{23}(t) = U\sqrt{2} \cdot \sin\left(\omega t - \frac{\pi}{2}\right) \\ U_{32}(t) = U\sqrt{2} \cdot \sin\left(\omega t - \frac{7\pi}{6}\right) \end{cases}$	$\cos \frac{\pi}{6} = \frac{U}{2V} = \frac{\sqrt{3}}{2}$ $U = \sqrt{3} \cdot V$
<ul style="list-style-type: none"> <li>✓ Three-phase receivers: are receivers made up of three identical impedance dipoles <math>\underline{Z}</math></li> <li>✓ Balanced because the three elements are identical</li> <li>✓ <math>\underline{I}</math> : Per-phase currents are the currents flowing through the <b>loads</b> <math>\underline{Z}</math> of the three-phase receiver</li> <li>✓ <math>\underline{I}</math> : Line currents are the currents that flow through the <b>wires</b> of the three-phase network</li> </ul>	


### a) Balanced wye-connection.(Y)

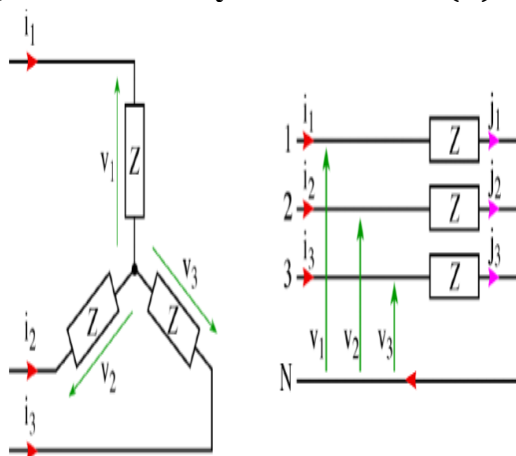

•  $I_i = I_i$

The relationship between simple and compound voltages is:

### b) Balanced delta connection (Δ)

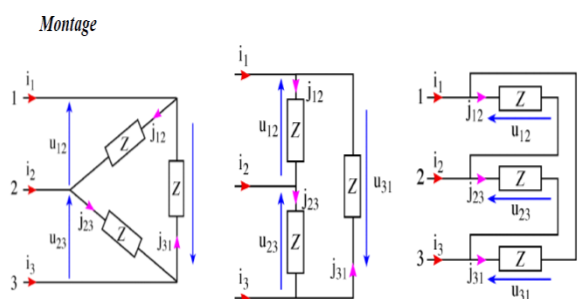


Même branchement représenté de trois façons différentes.  
Le premier schéma explique le terme « triangle ».

Symbole :  $\triangle$


Each phase of the receiver is subjected to a compound voltage  $\underline{U}_{ij}$  et  $i \neq j$

$$U_{ij}(t) = V_i(t) - V_j(t)$$

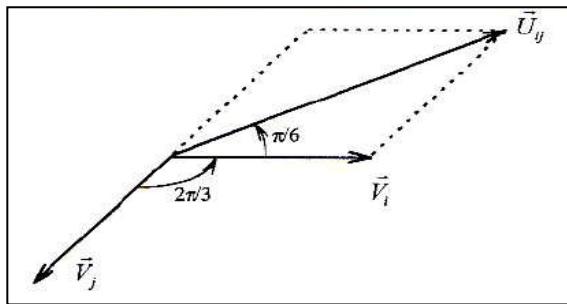

\*\*\*\*\*
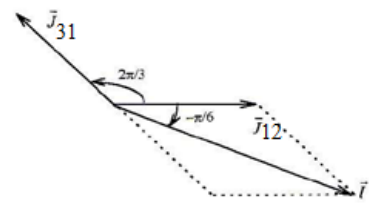
$$= \frac{\sqrt{3}}{2} \frac{V_i}{Z} e^{j\pi/6}$$



$$\begin{aligned} I_1 &= I_{12} - I_{31} \\ I_2 &= I_{23} - I_{12} \\ I_3 &= I_{31} - I_{23} \end{aligned}$$

$$I_{12} = \frac{U_{12}}{Z}; \quad I_{23} = \frac{U_{23}}{Z}; \quad I_{31} = \frac{U_{31}}{Z}$$

$$\text{So in effective value: } I_{12} = I_{23} = I_{31} = \frac{U}{Z}$$

The above diagram leads to the complex relationship:

$$I_i = \sqrt{3} I_{ij} e^{-j\pi/6} \quad \text{*****}$$

### III / Three-phase powers

In the case of a balanced system, the active and reactive powers are the same on each phase, so it is sufficient to reason on the single-phase equivalent diagram and multiply the power per phase by the number 3.

#### 1. Powers for wye connecting:

Pour une phase du récepteur :

$$P_1 = VI \cos \varphi$$

avec  $\varphi (I, V)$

Pour le récepteur complet :

$$P = 3.P_1 = 3VI \cos \varphi$$

de plus  $V = \frac{U}{\sqrt{3}}$

Finalement pour le couplage étoile :

$$P = \sqrt{3}UI \cos \varphi$$

de la même façon :

$$Q = \sqrt{3}UI \sin \varphi$$

et :

$$S = \sqrt{3}UI$$

Facteur de puissance :

$$FP = \cos \varphi$$

#### 2. Powers for a triangle connecting

Pour une phase du récepteur :

$$P_1 = UJ \cos \varphi$$

avec  $\varphi (J, U)$

Pour le récepteur complet :

$$P = 3.P_1 = 3UJ \cos \varphi$$

de plus  $J = \frac{I}{\sqrt{3}}$

Finalement pour le couplage étoile :

$$P = \sqrt{3}UI \cos \varphi$$

de la même façon :

$$Q = \sqrt{3}UI \sin \varphi$$

et :

$$S = \sqrt{3}UI$$


Facteur de puissance :

$$FP = \cos \varphi$$

### 3. Three-phase power measurements
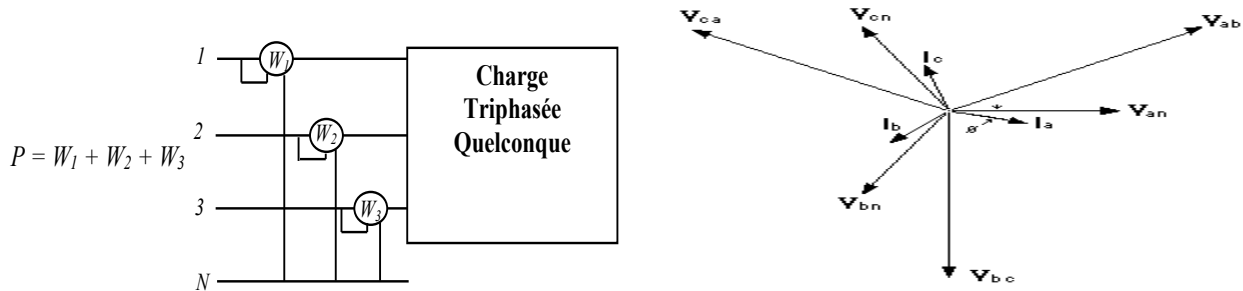
#### a) General method called "three Wattmeters method"

As the system has three phases, each consuming its own power, it is necessary to have 3 wattmeters to measure the total power.




- **Disadvantages:**

Requires the presence of neutral (therefore triangle assembly excluded) and use of 3 wattmeters

- **Advantage :** works regardless of load.
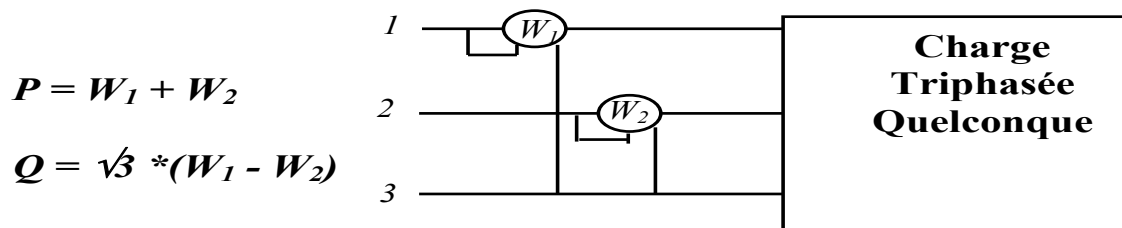
#### b) Two Wattmeter Method

We arrange the 2 wattmeters, as shown in the diagram below:



#### Démonstration :

- $W_1 + W_2 = \langle (v_1 - v_3)(t) \cdot i_1(t) + (v_2 - v_3)(t) \cdot i_2(t) \rangle = \langle v_1(t) \cdot i_1(t) + v_2(t) \cdot i_2(t) + v_3(t) \cdot (-i_1(t) - i_2(t)) \rangle$

We know that if the system is balanced or unbalanced without a neutral,  $i_1(t) + i_2(t) + i_3(t) = 0$ . So :

$$\boxed{W_1 + W_2 = P_{\text{total}}}$$

- $W_1 = \langle (v_1 - v_3) \cdot i_1(t) \rangle = V \cdot I \cdot \cos(\varphi - \pi/6)$
- $W_2 = \langle (v_2 - v_3) \cdot i_2(t) \rangle = V \cdot I \cdot \cos(\varphi + \pi/6)$

so

$$W_1 - W_2 = -2 \cdot V \cdot I \cdot \sin\varphi \cdot \sin(-\pi/6) = Q_{\text{total}}/\sqrt{3}$$

#### -Disadvantages:

- **Conditions of validity:**  $P = W_1 + W_2$  is only true if the system is balanced or unbalanced without a neutral.
- $Q = -3(W_1 - W_2)$  is only true if the system is balanced.

#### -Advantage :

requires only 2 wattmeters or a single wattmeter with a switch

